

# 11 - Broadband Amplifiers

The information in this work has been obtained from sources believed to be reliable.  
The author does not guarantee the accuracy or completeness of any information  
presented herein, and shall not be responsible for any errors, omissions or damages  
as a result of the use of this information.

August 2007

© 2007 Fabian Kung Wai Lee

1

## References

- [1]\* G. Gonzalez, "Microwave transistor amplifiers - analysis and design", 2nd Edition 1997, Prentice-Hall.
- [2] D. M. Pozar, "Microwave engineering", 2nd Edition, 1998 John-Wiley & Sons.
- [3] G. D. Vendelin, A. M. Pavio, U. L. Rohde, "Microwave circuit design - using linear and nonlinear techniques", 1990, John-Wiley & Sons.

August 2007

© 2007 Fabian Kung Wai Lee

2

## Introduction

- Up to now we have been looking at amplifier design at one frequency or over a narrow band of frequencies centered at  $f_c$ . Narrow band in this context implies 5% of  $f_c$  or smaller.
- In this section we will review broadband amplifier design.
- Some issues related to broadband amplifier design:
  - S-parameters of a transistor are dependent on frequency. Typically  $S_{21}$  decrease at a rate of 20dB/decade as frequency increase.
  - There is a degradation of noise figure and VSWR in some frequency range of the amplifier.
- Basically the design of a constant-gain amplifier over a broad frequency range is a matter of properly designing the matching networks, or feedback network to compensate for the variation of S-parameters with frequency.

August 2007

© 2007 Fabian Kung Wai Lee

3

## Typical Methods of Achieving Broadband Operation

- (1) The use of compensated impedance matching networks.
- (2) The use of negative feedback.
- (3) Combining either (1) or (2) with the balanced design approach.

August 2007

© 2007 Fabian Kung Wai Lee

4

# 1.0 Compensated Impedance Matching

August 2007

© 2007 Fabian Kung Wai Lee

5

## Compensated Impedance Matching (1)

- A strategy of designing wideband amplifier using compensated impedance matching approach is to examine the expression for the transducer power gain.

$$G_T = \frac{(1 - |\Gamma_L|^2) |S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{22}\Gamma_L|^2 |1 - \Gamma_L\Gamma_s|^2} \quad (1.1)$$

- If we enforce  $\Gamma_s = 0$  (i.e. make  $Z_s = Z_o$ ), then

$$G_{TL} = \frac{(1 - |\Gamma_L|^2) |S_{21}|^2}{|1 - S_{22}\Gamma_L|^2} \quad (1.2)$$

- A wideband impedance transformation network can then be designed to transform the load impedance  $Z_L$  so that  $\Gamma_L$  fulfills (1.2) within the operating frequency band.

August 2007

© 2007 Fabian Kung Wai Lee

6

## Compensated Impedance Matching (2)

- For a fixed  $G_T$ , the values of  $\Gamma_L$  which fulfills (1.2) is a circle on the Smith chart. First we write (1.2) as:

$$\frac{G_{TL}(1-|S_{22}|^2)}{|S_{21}|^2} = g_L = \frac{(1-|\Gamma_L|^2)(1-|S_{22}|^2)}{|1-S_{22}\Gamma_L|^2}$$

- Following the procedures as outlined in Chapter 11, Pozar [2], this can be expanded as:

$$|\Gamma_s - T_{G_{TL}}|^2 = R_{G_{TL}}^2 \quad (1.3a)$$

$$T_{G_{TL}} = \frac{g_L \operatorname{Re}(S_{22}^*)}{1-(1-g_L)|S_{22}|^2} + j \frac{g_L \operatorname{Im}(S_{22}^*)}{1-(1-g_L)|S_{22}|^2} \quad (1.3b)$$

$$R_{G_{TL}} = \frac{\sqrt{1-g_L}(1-|S_{22}|^2)}{1-(1-g_L)|S_{22}|^2} \quad (1.3c)$$

August 2007

© 2007 Fabian Kung Wai Lee

7

## Compensated Impedance Matching (3)

- A few constant constant  $G_{TL}$  circles will be plotted on the Smith chart for  $\Gamma_L$  at different frequencies.
- From these circles, suitable values of  $Z_L'$  will be identified at each frequency and a wideband impedance transformation network is designed to transform the actual load impedance  $Z_L$  to  $Z_L'$  at the designated frequency.
- Usually computer optimization method is needed for this procedure.
- An example will serve to illustrate this concept.


August 2007

© 2007 Fabian Kung Wai Lee

8

## Example 1 - Wideband Amplifier Design with ADS Software Using Compensated Impedance Matching Method

- In this exercise, an attempt is made to design a wideband amplifier using compensated impedance transformation technique. The active device used is Phillips' BFR92A bipolar junction transistor.
- The intention is to design an amplifier with a transducer gain  $G_T = 30$  (14.77dB) under the condition shown, with a bandwidth from 350MHz to 450MHz.

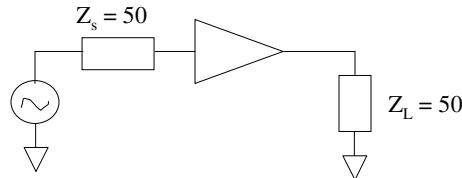


August 2007

© 2007 Fabian Kung Wai Lee

9

## Example 1 Cont...

- As a start the following CE amplifier is constructed. DC analysis and S-parameter analysis are performed.

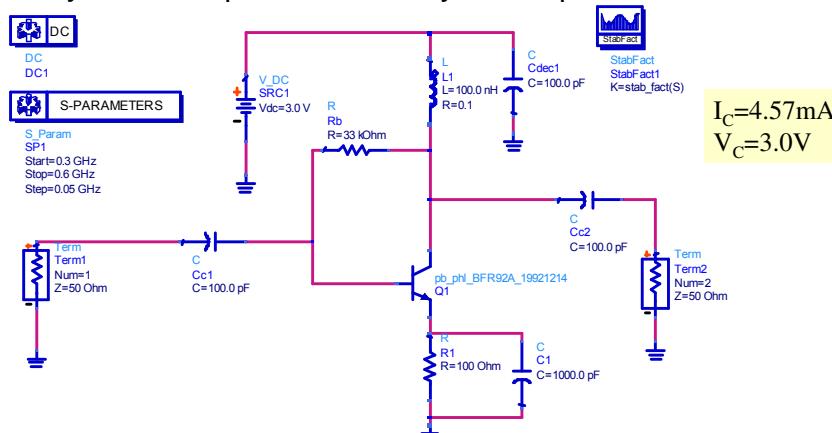

August 2007


© 2007 Fabian Kung Wai Lee

10

## Example 1 Cont...

- From the magnitude of  $S_{21}$ , it is evident that this circuit can provide  $G_T$  in excess of 30 when  $\Gamma_s = \Gamma_L = 0$  ( $Z_L = Z_s = Z_o = 50$ ).

freq	$S(1,1)$	$S(2,1)$	$S(1,2)$	$S(2,2)$	K
300.0MHz	0.588 / -73.754	9.147 / 136.949	0.057 / 74.493	0.618 / 3.223	0.572
350.0MHz	0.526 / -80.718	8.200 / 128.933	0.063 / 72.276	0.579 / -1.616	0.654
400.0MHz	0.475 / -95.913	7.405 / 122.439	0.097 / 70.975	0.547 / -4.954	0.724
450.0MHz	0.432 / -92.545	6.789 / 117.022	0.072 / 70.246	0.522 / -7.340	0.784
500.0MHz	0.396 / -97.756	6.174 / 112.393	0.077 / 69.877	0.502 / -9.105	0.855
550.0MHz	0.366 / -102.652	5.693 / 108.360	0.082 / 69.730	0.485 / -10.458	0.878
600.0MHz	0.340 / -107.305	5.280 / 104.785	0.087 / 69.716	0.471 / -11.533	0.914

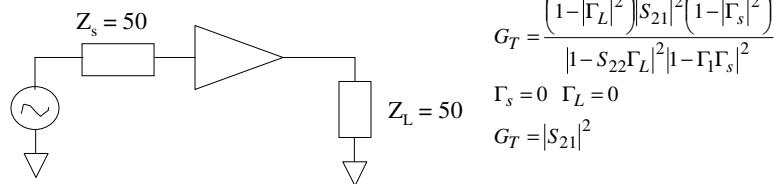


August 2007

© 2007 Fabian Kung Wai Lee

11

## Example 1 Cont...

- A plot of  $G_T$  versus frequency is shown below. Note that the transducer power gain varies greatly from around 65 to 45 over the intended operating frequency range.

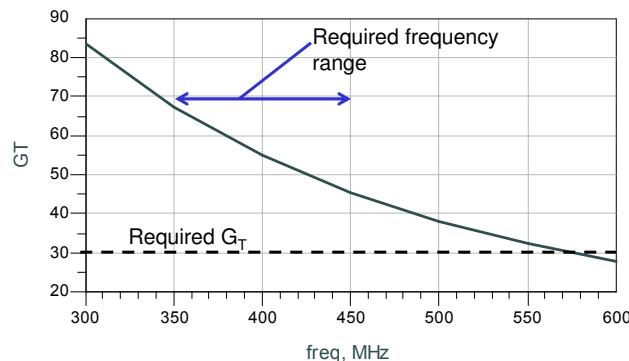

August 2007

© 2007 Fabian Kung Wai Lee

12

## Example 1 Cont...

- Equations (1.3b) & (1.3c) are used to find the center and radius corresponds to constant  $G_T$  circle ( $G_T = 30$ ). The macros below are used in the ADS's data display for this purpose.

```

Eqn GTL=30      Eqn Zo=50
Eqn gL=(GTL*(1-pow(mag(S(2,2)),2))/pow(mag(S(2,1)),2))
Eqn TGTL=gL*conj(S(2,2))/(1-(1-gL)*pow(mag(S(2,2)),2))
Eqn RGTL=(sqrt(1-gL)*(1-pow(mag(S(2,2)),2)))/(1-(1-gL)*pow(mag(S(2,2)),2))

```

```

Eqn theta=generate(0,2*pi,201)
Eqn Circle_GTL0=RGTL[1]*exp(j*theta)+TGTL[1] ← Circle for 350MHz
Eqn Circle_GTL1=RGTL[2]*exp(j*theta)+TGTL[2] ← Circle for 400MHz
Eqn Circle_GTL2=RGTL[3]*exp(j*theta)+TGTL[3] ← Circle for 450MHz

```


August 2007

© 2007 Fabian Kung Wai Lee

13
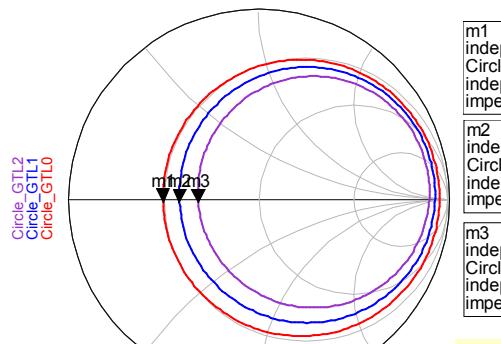
## Example 1 Cont...

- 3 constant  $G_{TL}$  circles are plotted, for  $f = 350\text{MHz}$ ,  $400\text{MHz}$  and  $450\text{MHz}$ . 3 convenient points as shown are chosen for the required  $\Gamma_L$ .



m1	indep
Circle	Circ
GTL2	indep

m2	indep
Circle	Circ
GTL1	indep

m3	indep
Circle	Circ
GTL0	indep

$$\begin{aligned}
 Z_{L(350\text{MHz})} &= 16.45+j0 \\
 Z_{L(400\text{MHz})} &= 20.55+j0 \\
 Z_{L(450\text{MHz})} &= 25.85+j0
 \end{aligned}$$


August 2007

© 2007 Fabian Kung Wai Lee

14

## Example 1 Cont...

- A pi network network is then proposed as the impedance transformation network that would give the required  $Z_L$  at  $f = 350\text{MHz}$ ,  $400\text{MHz}$ , and  $450\text{MHz}$ .
- NOTE: A pi network is proposed as we have 3 variables in the pi network ( $C_1$ ,  $C_2$  and  $L_1$ ) and 3 degrees of freedom. This bodes well with 3 constraints as determined by the real values of  $Z_L$  at  $350\text{MHz}$ ,  $400\text{MHz}$  and  $450\text{MHz}$ .
- Optimization is carried out to find the best values for  $C_1$ ,  $C_2$  and  $L_1$  that will do the job. The optimization control with the associated goal functions are shown in the next slide.

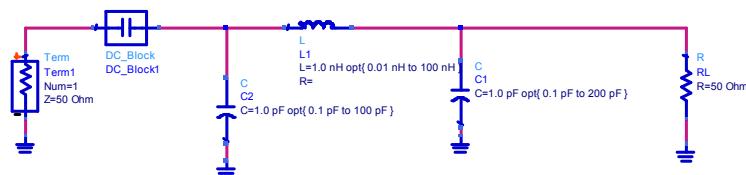

August 2007

© 2007 Fabian Kung Wai Lee

15

## Example 1 Cont...

S-PARAMETERS	GOAL	GOAL
<pre> S_Param SP1 Start=0.35 GHz Stop=0.45 GHz Step=0.05 GHz </pre>	<pre> Goal OptimGoal1 Expr="mag(real(S11)-(-0.505))" SimInstanceName="SP1" Min= Max=0.02 Weight= RangeVar[1]="freq" RangeMin[1]=350MHz RangeMax[1]=350MHz </pre>	<pre> Goal OptimGoal2 Expr="mag(real(S11)-(-0.418))" SimInstanceName="SP1" Min= Max=0.02 Weight= RangeVar[1]="freq" RangeMin[1]=400MHz RangeMax[1]=400MHz </pre>
<pre> OPTIM Optim OptimType=Gradient UseAllGoals=yes ErrorForm=L2 MaxIters=200 DesiredError=0.0 StatusLevel=4 FinalAnalysis="None" SetBestValues=yes Seed= SaveSols=no SaveGoals=yes SaveOptimVars=no UpdateDataset=yes SaveNominal=yes SaveAllIterations=no UseAllOptVars=yes </pre>	<pre> GOAL Goal OptimGoal3 Expr="pow(imag(S11),2)" SimInstanceName="SP1" Min= Max=0.02 Weight= RangeVar[1]="freq" RangeMin[1]=450MHz RangeMax[1]=450MHz </pre>	<pre> GOAL Goal OptimGoal4 Expr="pow(imag(S11),2)" SimInstanceName="SP1" Min= Max=0.02 Weight= RangeVar[1]="freq" RangeMin[1]=350MHz RangeMax[1]=450MHz </pre>

August 2007

© 2007 Fabian Kung Wai Lee

16

## Example 1 Cont...

- The transformed load impedance using the pi network.

The optimized results, after 12 iterations

NumIters	InitialEF	FinalEF	C1.C	C2.C	L1.L
12.000	0.450	0.000	1.270E-11	1.087E-11	1.249E-8

freq	S(1,1)	Z(1,1)
300.0MHz	0.507 / -159.704	16.842 - j7.962
350.0MHz	0.492 / -171.119	17.123 - j3.430
400.0MHz	0.438 / 175.056	19.569 + j1.828
450.0MHz	0.330 / 155.187	26.082 + j8.109
500.0MHz	0.163 / 110.351	42.688 + j13.418

Compare these with the requirements


August 2007

© 2007 Fabian Kung Wai Lee

17

## Example 1 Cont...

- Finally, the pi network is incorporated into the original circuit, and an S-parameter analysis is performed to verified the performance of the complete circuit.

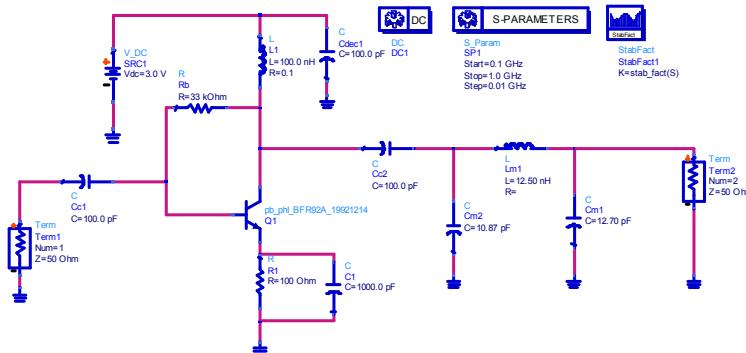


August 2007

© 2007 Fabian Kung Wai Lee

18

## Example 1 Cont...

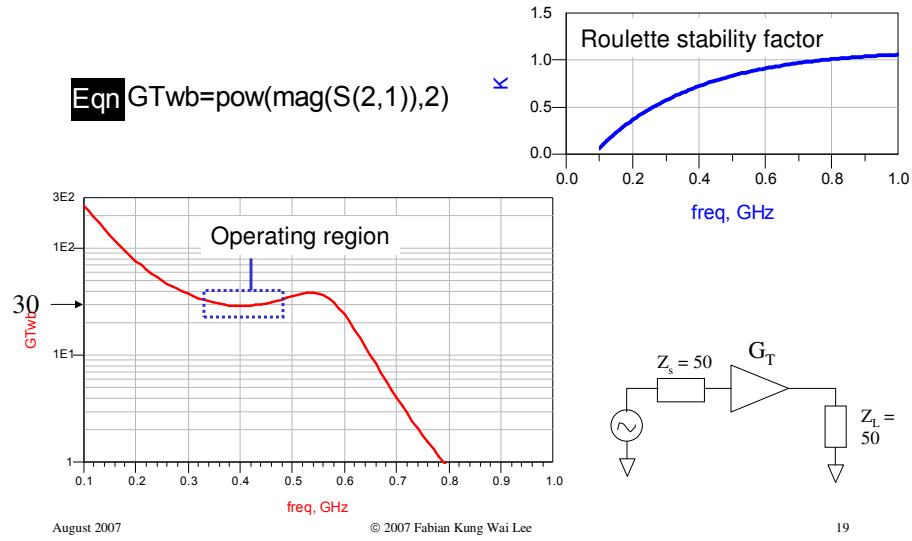

## Drawbacks of this Approach

- Usually is limited to bandwidth of 1 decade.
- Considerable ripple is present within the operating bandwidth.
- The design of the required impedance transformation network is more of an art, largely a hit or miss affair.
- Power gain is not optimized, as seen in this example, there is large amount of mismatch at the input and output. Power gain is sacrificed at the expense of wideband operation.

## 2.0 Negative Feedback

August 2007

© 2007 Fabian Kung Wai Lee

21

### Negative Feedback

- Negative feedback is widely used in amplifier design for the following reasons:
  - Negative feedback stabilizes the gain of the amplifier against parameter changes in the active device due to voltage variation, temperature drift or device aging.
  - To increase the bandwidth of the amplifier (at the expense of maximum gain).
  - To improve the gain linearity of an amplifier.
  - To change the input and output impedance of the amplifier.
- For a detailed discussion on negative feedback, please refer to chapter 8 of Gray & Meyer [2].


August 2007

© 2007 Fabian Kung Wai Lee

22

## Negative Feedback Review (1)

**Extra**

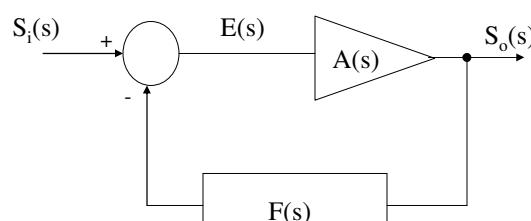

$$\frac{S_o}{S_i}(s) = G(s) = \frac{A(s)}{1 + A(s)F(s)}$$

Closed-loop gain (2.1)

$$T(s) = A(s)F(s)$$

Loop gain (2.2)

Properties of  $G(s)$ :

$$\frac{\Delta G(s)}{G(s)} = \frac{\Delta A(s)}{1 + T(s)} \quad \text{Stabilization of gain against parameter variation}$$

If  $T(s) \gg 1 \rightarrow \frac{S_o}{S_i}(s) \approx \frac{1}{F(s)}$


August 2007

© 2007 Fabian Kung Wai Lee

23

## Negative Feedback Review (2)

**Extra**

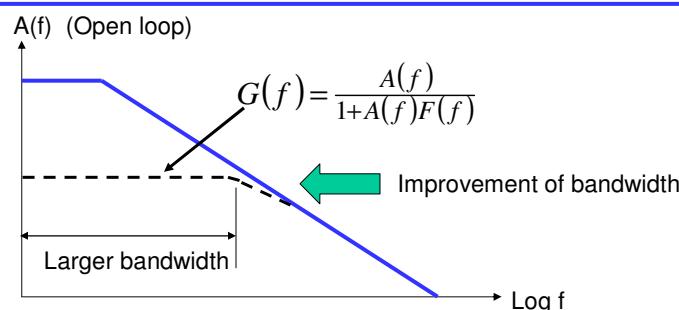


- 4 basic configurations of feedback system:
  - Shunt-shunt feedback.
  - Shunt-series feedback.
  - Series-shunt feedback.
  - Series-series feedback.

August 2007

© 2007 Fabian Kung Wai Lee

24
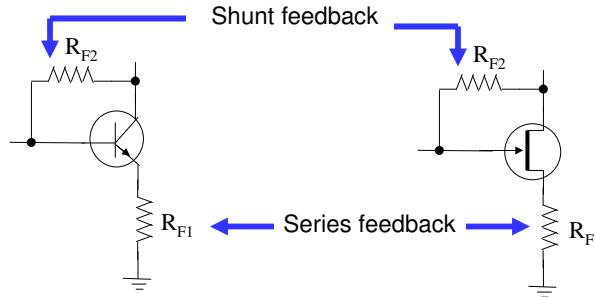
## Implementing Local Negative Feedback on Transistor and FET



The shunt and series feedback can be implemented separately or together.


August 2007

© 2007 Fabian Kung Wai Lee

25


## More on Local Feedbacks on Transistor and FET

Only shunt feedback:

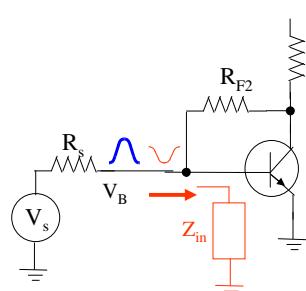

For detailed analysis see Chapter 8,  
Gray & Meyer [2]

Output voltage is shifted by 180°

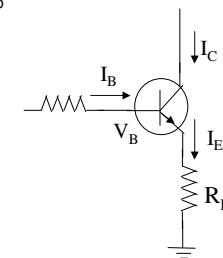

Only series feedback:


$$I_C + i_c = I_{se} e^{\frac{(V_B + v_b) - (V_E + v_e)}{V_T} - 1}$$

$$I_C + i_c = I_{se} e^{\frac{(V_B - V_E) + (v_b - v_e)}{V_T} - 1}$$

$$I_C + i_c \approx I_{se} e^{\frac{(V_B - V_E)}{V_T} e^{\frac{(v_b - v_e)}{V_T}}}$$

$$\Rightarrow i_c \approx \left( \frac{I_C}{V_T} \right) (v_b - v_e)$$

$$\Rightarrow i_c \approx \left( \frac{I_C}{V_T} \right) (v_b - i_c R_F1)$$

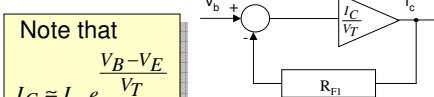

August 2007



© 2007 Fabian Kung Wai Lee

26

Note that

$$I_C \approx I_{se} e^{\frac{V_B - V_E}{V_T}}$$
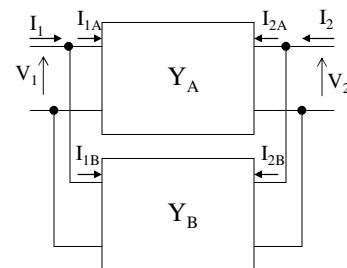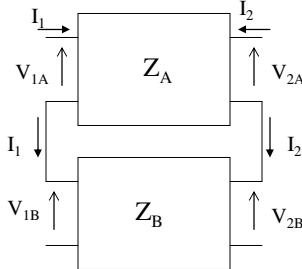
## Using Y and Z Parameters with Feedback (1)



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_{1A} \\ V_{2A} \end{bmatrix} + \begin{bmatrix} V_{1B} \\ V_{2B} \end{bmatrix} = (\bar{Z}_A + \bar{Z}_B) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad (2.3a)$$

Series Feedback

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{1A} \\ I_{2A} \end{bmatrix} + \begin{bmatrix} I_{1B} \\ I_{2B} \end{bmatrix} = (\bar{Y}_A + \bar{Y}_B) \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad (2.3b)$$


Shunt Feedback

August 2007


© 2007 Fabian Kung Wai Lee

27
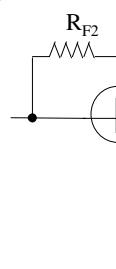
## Using Y and Z Parameters with Feedback (2)



Z matrix for BJT

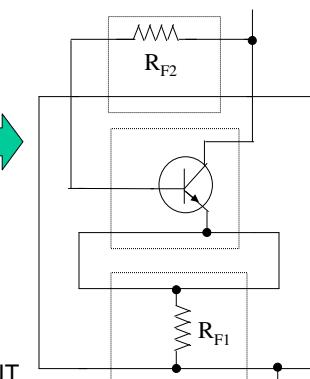

$$\bar{Y} = \begin{bmatrix} \frac{1}{R_{F2}} & \frac{-1}{R_{F2}} \\ \frac{-1}{R_{F2}} & \frac{1}{R_{F2}} \end{bmatrix} \quad (2.4a)$$

$$\bar{Z} = \begin{bmatrix} R_{F1} & R_{F1} \\ R_{F1} & R_{F1} \end{bmatrix} \quad (2.4b)$$

$$\begin{aligned} S_{11t} &= \frac{(Y_o - y_{11})(Y_o + y_{22}) + y_{12}y_{21}}{\Delta y} \\ S_{12t} &= \frac{-2y_{12}Y_o}{\Delta y} \\ S_{21t} &= \frac{-2y_{21}Y_o}{\Delta y} \\ S_{22t} &= \frac{(Y_o + y_{11})(Y_o - y_{22}) + y_{12}y_{21}}{\Delta y} \\ \Delta y &= (Y_o + y_{11})(Y_o + y_{22}) - y_{12}y_{21} \end{aligned} \quad (2.4c)$$

$$\bar{Y}_t = \left\{ \begin{bmatrix} R_{F1} & R_{F1} \\ R_{F1} & R_{F1} \end{bmatrix} + \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \right\}^{-1} + \begin{bmatrix} \frac{1}{R_{F2}} & \frac{-1}{R_{F2}} \\ \frac{-1}{R_{F2}} & \frac{1}{R_{F2}} \end{bmatrix} \quad (2.4c)$$

Using Y to S matrix transformation  $\bar{S}_{total}$


August 2007

© 2007 Fabian Kung Wai Lee

28
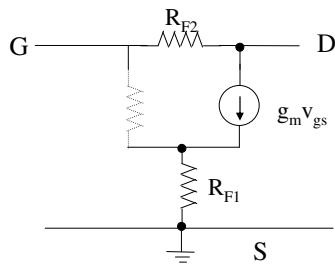
## Simplified Low-Frequency Feedback Analysis (1)

- The following derivation is taken from Chapter 4 of Gonzalez [1]. Consider a low frequency FET model with feedback:



This is also applicable to BJT provided:

$$r_{be} + h_{fe}R_{F1} \gg R_{F2} \quad (2.7)$$

The  $Y_t$  matrix can be easily derived:

$$\bar{Y}_t = \begin{bmatrix} \frac{1}{R_{F2}} & \frac{-1}{R_{F2}} \\ \frac{g_m}{1+g_m R_{F1}} + \frac{-1}{R_{F2}} & \frac{1}{R_{F2}} \end{bmatrix} \quad (2.5)$$

And converted to S-parameter:

$$\begin{aligned} S_{11t} &= S_{22t} = \frac{1}{D} \left[ 1 - \frac{g_m Z_o^2}{R_{F2}(1+g_m R_{F1})} \right] \\ S_{21t} &= \frac{1}{D} \left( \frac{-2g_m Z_o}{1+g_m R_{F1}} + \frac{2Z_o}{R_{F2}} \right) \\ S_{12t} &= \frac{2Z_o}{DR_2} \\ D &= 1 + \frac{2Z_o}{R_{F2}} + \frac{g_m Z_o^2}{R_{F2}(1+g_m R_{F1})} \end{aligned} \quad (2.6)$$

August 2007

© 2007 Fabian Kung Wai Lee

29

## Simplified Low-Frequency Feedback Analysis (2)

- If we require that:

$$1 + g_m R_{F1} = \frac{g_m Z_o^2}{R_{F2}} \quad \rightarrow \quad R_{F1} = \frac{Z_o^2}{R_{F2}} - \frac{1}{g_m} \quad (2.8)$$

- Then  $S_{11t} = S_{22t} = 0$

$$S_{21t} = \frac{Z_o - R_{F2}}{Z_o} \quad (2.9b)$$

$$S_{12t} = \frac{Z_o}{Z_o + R_{F2}} \quad (2.9c)$$

- In the case when only shunt feedback is applied ( $R_{F1} = 0$ ):

$$\frac{1}{g_m} = \frac{Z_o^2}{R_{F2}} \quad (2.10a)$$

$$R_{F2} = Z_o (1 - S_{21}) \quad (2.10b)$$

For BJT additional requirement:

$$r_{be} \gg R_{F2}$$


Observe that S-parameters is no longer dependent on active device parameter

August 2007

© 2007 Fabian Kung Wai Lee

30
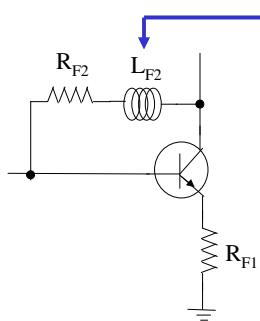
## Typical Local Negative Feedbacks on Transistor and FET at RF



- At high frequency, phase difference between voltage at collector and base will be less than  $180^\circ$ . Instead of negative feedback, this could lead to positive feedback, resulting in instability.  $L_{F2}$  is used to introduce  $90^\circ$  phase lead when the phase difference between C and B is less than  $90^\circ$ .
- The phase difference information can be obtained from  $S_{21}$ .

August 2007

© 2007 Fabian Kung Wai Lee

31

## Design Equations for Negative Feedback Amplifier

- In general to implement local feedback on BJT or FET, we begin with the low frequency design.
- Equations (2.8) and (2.9b) are used to find the approximate values for  $R_{F1}$  and  $R_{F2}$ .
 
$$R_{F1} = \frac{Z_o^2}{R_{F2}} - \frac{1}{g_m}$$

$$S_{21t} = \frac{Z_o - R_{F2}}{Z_o}$$
- In the low frequency model  $S_{21}$  is negative (e.g.  $180^\circ$  phase shift), hence (2.9b) can be written as:
 
$$R_{F2} = Z_o(1 + |S_{21t}|) \quad (2.11)$$
- Since at high frequency parasitic capacitance and inductance effect become evident, CAD software is then used to fine tune the resistor values to obtain good input/output VSWR (i.e.  $S_{11t}$  and  $S_{22t}$  close to 0) and fairly constant  $S_{21t}$  and  $S_{12t}$  as a function of frequency.

$$\omega_l L_{F2} = R_{F2} \quad (2.12)$$

$\omega_l$  = frequency where  $S_{21}$  of active device phase is less than  $90^\circ$

August 2007

© 2007 Fabian Kung Wai Lee

32

## Example 2 - Negative Feedback Amplifier Design Example with ADS Software


- In this exercise, an attempt is made to design a wideband amplifier using negative feedback technique. The active device used is BFR92A bipolar junction transistor.
- The objectives:
  - To stabilize  $|S_{21t}|$  to around 3.2 between 100MHz-1000MHz.
  - $S_{11t}$  and  $S_{22t}$  close to zero within the same frequency range.

August 2007

© 2007 Fabian Kung Wai Lee

33

## Example 2 Cont...

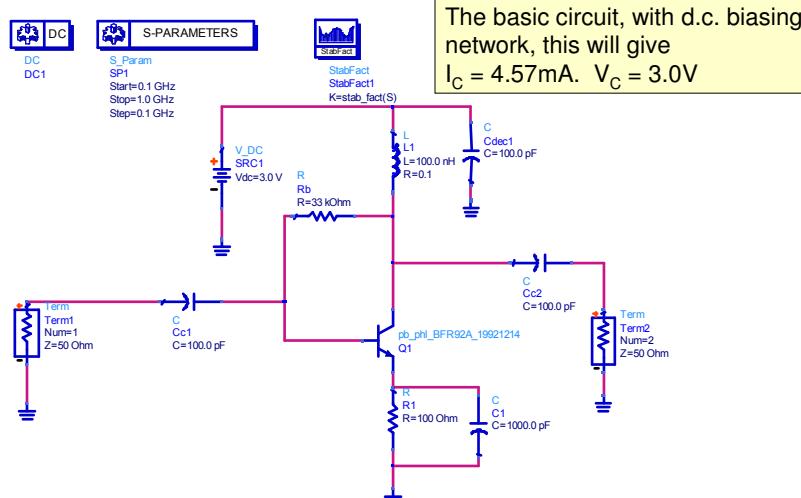

August 2007

© 2007 Fabian Kung Wai Lee

34

## Example 2 Cont...

- The S-parameters for the basic circuit:

freq	S(1,1)	S(2,1)	S(1,2)	S(2,2)	K
100.0MHz	0.953 / -30.336	13.323 / -145.899	0.026 / 115.045	0.885 / 79.968	0.061
200.0MHz	0.753 / -56.236	11.532 / 161.011	0.045 / 84.359	0.729 / 22.013	0.364
300.0MHz	0.588 / -73.754	9.147 / 136.949	0.057 / 74.493	0.618 / 3.223	0.572
400.0MHz	0.475 / -86.913	7.406 / 122.439	0.067 / 70.975	0.547 / -4.954	0.724
500.0MHz	0.396 / -97.756	6.174 / 112.393	0.077 / 69.877	0.502 / -9.105	0.835
600.0MHz	0.340 / -107.305	5.280 / 104.785	0.087 / 69.716	0.471 / -11.533	0.914
700.0MHz	0.300 / -116.087	4.609 / 98.647	0.097 / 69.880	0.449 / -13.181	0.971
800.0MHz	0.270 / -124.378	4.092 / 93.464	0.108 / 70.105	0.432 / -14.467	1.011
900.0MHz	0.247 / -132.318	3.683 / 88.937	0.119 / 70.282	0.418 / -15.589	1.040
1.000GHz	0.231 / -139.963	3.353 / 84.881	0.130 / 70.365	0.407 / -16.647	1.059

$S_{21}$  has magnitude > 3.2 from 100MHz to 1000MHz. Also note that the phase is less than 90° beginning from 700MHz. So we choose

$$S_{21(\text{feedback})} = 3.2$$

Note a small K stability factor indicates the basic amplifier is less stable at the low frequency range.

August 2007

© 2007 Fabian Kung Wai Lee

35

## Example 2 Cont...

- Finding the low frequency approximation values for  $R_{F1}$ ,  $R_{F2}$  and approximation for  $L_{F2}$ .

$$R_{F2} = Z_o (1 + |S_{21t}|) = 50(1 + 3.2) = 210\Omega$$

$$g_m = \left( \frac{I_C}{\frac{kT}{q}} \right) \cong \frac{0.00457}{0.026} = 0.1758$$

$$R_{F1} = \frac{Z_o^2}{R_{F2}} - \frac{1}{g_m} = 6.22\Omega$$

$$L_{F2} = \frac{R_{F2}}{2\pi f_1} = 47.75nH$$

$$f_1 = 700MHz$$


August 2007

© 2007 Fabian Kung Wai Lee

36

## Example 2 Cont...

Feedback network is added. Tuning is carried to optimize the S-parameters of the resulting amplifier. The final values:  
 $R_{F1} = 270 \text{ Ohm}$   
 $R_{F2} = 2.2 \text{ Ohm}$   
 $L_{F2} = 33 \text{ nH}$   
A capacitor  $C_{f1}$  is added in series to act as d.c. block.

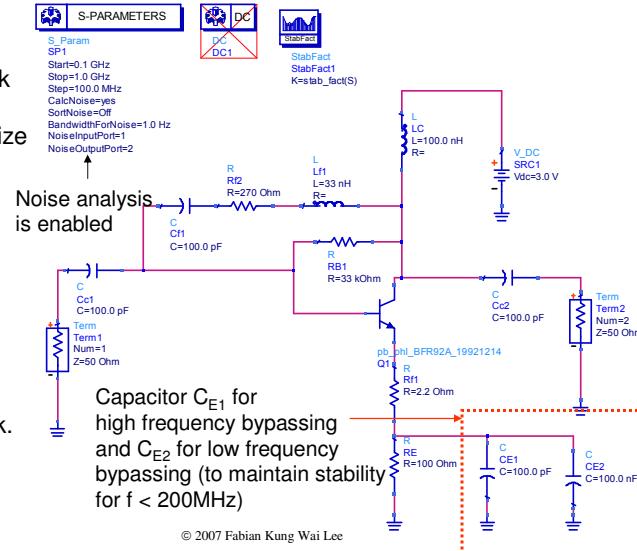

August 2007

37

## Example 2 Cont...

- The S-parameters for the amplifier with shunt and series feedback:

freq	S(2,1)	S(1,1)	S(2,2)	S(1,2)	K	mag(D)
100.0MHz	4.109 / -148.950	0.337 / -91.905	0.411 / 155.262	0.131 / 44.510	1.089	0.674
200.0MHz	4.311 / -177.298	0.162 / -118.464	0.329 / 117.327	0.139 / 24.522	1.072	0.645
300.0MHz	4.291 / 167.529	0.099 / -137.625	0.351 / 96.728	0.139 / 18.717	1.048	0.623
400.0MHz	4.233 / 156.688	0.066 / -152.510	0.391 / 81.187	0.139 / 16.460	1.026	0.607
500.0MHz	4.095 / 145.287	0.045 / -161.319	0.432 / 68.233	0.137 / 15.802	1.010	0.566
600.0MHz	3.943 / 136.786	0.032 / -160.105	0.467 / 56.973	0.134 / 16.295	1.008	0.532
700.0MHz	3.767 / 127.023	0.028 / -148.253	0.492 / 47.017	0.130 / 17.887	1.022	0.497
800.0MHz	3.575 / 118.951	0.032 / -137.738	0.508 / 38.172	0.127 / 20.582	1.050	0.463
900.0MHz	3.378 / 111.549	0.041 / -135.833	0.516 / 30.314	0.125 / 24.287	1.087	0.433
1.000GHz	3.183 / 104.787	0.051 / -139.405	0.517 / 23.338	0.125 / 28.744	1.126	0.408

Good matching to  $Z_o = 50$  for input

Magnitude of  $S_{21t}$  did not change much

Also note that because of feedback, the amplifier becomes unconditionally stable throughout the operating range.



August 2007

© 2007 Fabian Kung Wai Lee

38
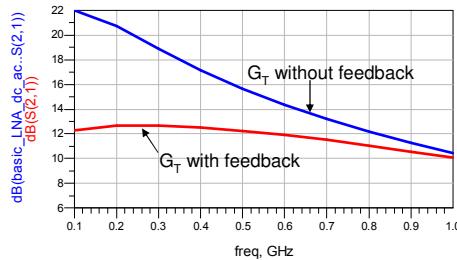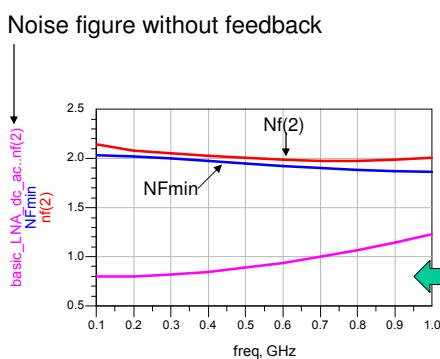
## Example 2 Cont...

- Plotting the transducer gain  $G_T$  with  $Z_s = Z_L = Z_0$ . Also plotted are the noise figure at output.



R<sub>F1</sub> and R<sub>F2</sub> degrade the noise performance slightly.

August 2007

© 2007 Fabian Kung Wai Lee

39

## 3.0 Balance Amplifier


August 2007

© 2007 Fabian Kung Wai Lee

40

## Balanced Amplifier

- The first 90° 3dB coupler divides the input signal into two equal-amplitude components with a 90° phase difference.
- The second 90° 3dB coupler recombines the amplifier outputs.
- Because of the phasing properties of the coupler, reflections from the amplifier inputs cancel at the input to the coupler, resulting in improved impedance match.
- A similar condition occurs at the output.

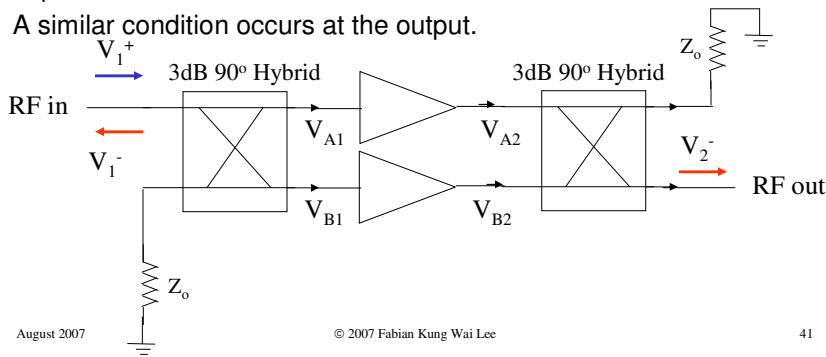

August 2007

© 2007 Fabian Kung Wai Lee

41

## Derivation of S-parameters for Balanced Amplifier (1)

- Assuming the 3dB hybrid couplers are ideal. Impedance looking into each port is equal to  $Z_o$ . Then:

$$\begin{aligned} V_{A1}^+ &= \frac{1}{\sqrt{2}} V_1^+ & V_{B1}^+ &= \frac{-j}{\sqrt{2}} V_1^+ \\ V_2^- &= \frac{-j}{\sqrt{2}} V_{A2}^+ + \frac{1}{\sqrt{2}} V_{B2}^+ = \frac{-j}{\sqrt{2}} S_{21A} V_{A1}^+ + \frac{1}{\sqrt{2}} S_{21B} V_{B1}^+ \\ &= \frac{-j}{2} V_1^+ (S_{21A} + S_{21B}) \end{aligned}$$

$$S_{21Balanced} = \frac{V_2^-}{V_1^+} = \frac{-j}{2} (S_{21A} + S_{21B}) \quad (3.1a)$$

- In a similar manner:

$$\begin{aligned} V_1^- &= \frac{1}{\sqrt{2}} V_{A1}^- + \frac{-j}{\sqrt{2}} V_{B1}^- = \frac{1}{\sqrt{2}} S_{11A} V_{A1}^+ + \frac{-j}{\sqrt{2}} S_{11B} V_{B1}^+ \\ &= \frac{1}{2} V_1^+ (S_{11A} - S_{11B}) \end{aligned}$$

$$S_{11Balanced} = \frac{V_1^-}{V_1^+} = \frac{1}{2} (S_{11A} - S_{11B}) \quad (3.1b)$$

August 2007

© 2007 Fabian Kung Wai Lee

42

## Derivation of S-parameters for Balanced Amplifier (2)

- If both amplifiers are equal:

$$S_{21A} = S_{21B} = S_{21} \quad S_{11A} = S_{11B} = S_{11}$$

- And

$$S_{21Balanced} = -jS_{21} \quad S_{11Balanced} = 0$$

- Finally, it can be shown that:

$$\bar{\bar{S}}_{Balanced} = \begin{bmatrix} 0 & -jS_{12} \\ -jS_{21} & 0 \end{bmatrix} \quad (3.2)$$

August 2007

© 2007 Fabian Kung Wai Lee

43

## Advantages of Balanced Amplifier

- The balanced amplifier has the following interesting advantages.
- The individual amplifier stages can be optimized for gain flatness or noise figure, without concern for input and output matching.
- Reflections are absorbed in the coupler terminations, improving input/output matching as well as stability of the individual amplifiers.
- Bandwidth greater than a decade or more can be achieved, primarily limited by the bandwidth of the coupler.
- The essence of wideband balanced amplifier – **Each amplifier itself must be wideband.**

August 2007

© 2007 Fabian Kung Wai Lee

44

## 射 频 和 天 线 设 计 培 训 课 程 推 荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立，致力并专注于微波、射频、天线设计研发人才的培养；我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com))，现已发展成为国内最大的微波射频和天线设计人才培养基地，成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程，广受客户好评；并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书，帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司，以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表：<http://www.edatop.com/peixun/rfe/129.html>

---



### 射频工程师养成培训课程套装


该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材；旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习，能够让学员完全达到和胜任一个合格的射频工程师的要求…

课程网址：<http://www.edatop.com/peixun/rfe/110.html>

---

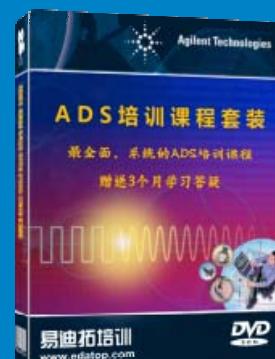
### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程，共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解，并多结合设计实例，由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS，迅速提升个人技术能力，把 ADS 真正应用到实际研发工作中去，成为 ADS 设计专家…



课程网址：<http://www.edatop.com/peixun/ads/13.html>

---

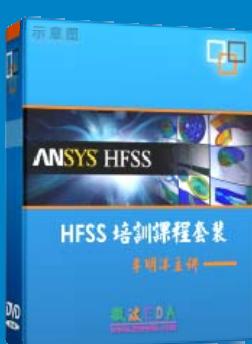

### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程，是迄今国内最全面、最专业的 HFSS 培训教程套装，可以帮助您从零开始，全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装，更可超值赠送 3 个月免费学习答疑，随时解答您学习过程中遇到的棘手问题，让您的 HFSS 学习更加轻松顺畅…

课程网址：<http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出，是最全面、系统、专业的 CST 微波工作室培训课程套装，所有课程都由经验丰富的专家授课，视频教学，可以帮助您从零开始，全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装，还可超值赠送 3 个月免费学习答疑…



课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书，课程从基础讲起，内容由浅入深，理论介绍和实际操作讲解相结合，全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程，可以帮助您快速学习掌握如何使用 HFSS 设计天线，让天线设计不再难…

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程，培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合，全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作，同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习，可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试…



详情浏览: <http://www.edatop.com/peixun/antenna/116.html>

## 我们的课程优势:

- ※ 成立于 2004 年，10 多年丰富的行业经验，
- ※ 一直致力并专注于微波射频和天线设计工程师的培养，更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授，结合实际工程案例，直观、实用、易学

## 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>