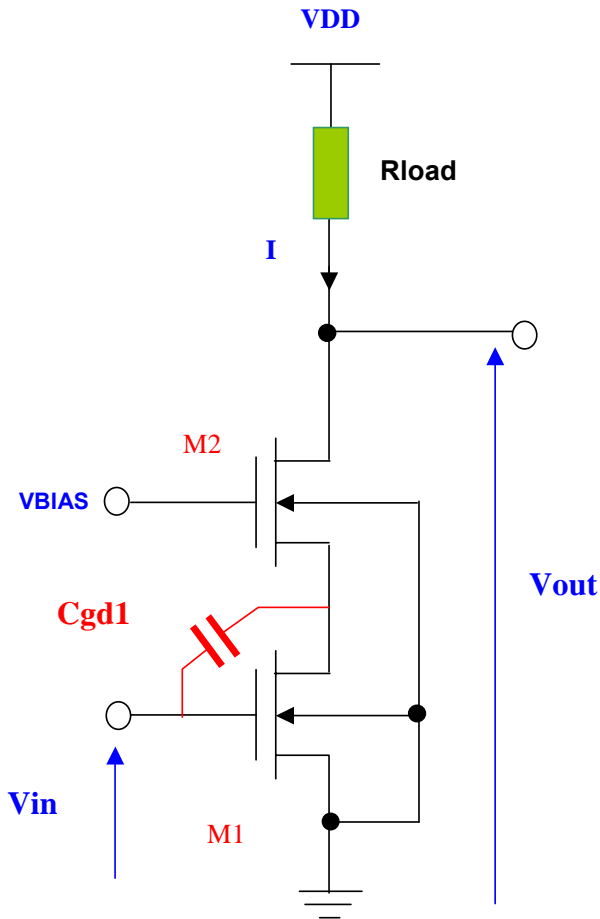


**Cascode CMOS Circuit**

The cascode is a combination of a common-source device with a common-gate load. This has the effect of increasing the output impedance but minimises the Miller effect making it an ideal configuration for use at high frequencies. The circuit of the cascode amplifier is shown in Figure 1.



**Figure 1 Basic Cascode Amplifier**

Lets assume that FET M2 has a short between the drain and source terminals, the remaining circuit will be a common-source amplifier with a gain of:

$$Av = gm_1 \cdot R_{LOAD} \text{ or } \frac{gm_1}{g_{load}} \text{ strictly speaking } Av = \frac{gm_1}{g_{o_{load}} + g_{o_1}}$$



Now miller effect occurs when there is a large impedance applied to the drain of the common-source M1 in this case it's  $R_{LOAD}$  but it could also be an active load with an even higher resistance. This has the effect of applying a gate shunt capacitance which, has a value of the M1 gate-drain capacitance multiplied by the voltage gain of the amplifier:-

$$C_{gate-shunt} = C_{gd1}(1 + (gm_1 \cdot R_{LOAD}))$$

Thus with a particular source impedance connected to the input of the amplifier the 3-dB break point will be:-

$$f_{3dB} = \frac{1}{2\pi \cdot R_s [C_{gs} + C_{gd1}(1 + (gm_1 \cdot R_{LOAD}))]}$$

If there is a load capacitor attached to the load then a second higher frequency pole will be introduced:

$$f_{3dB} = \frac{G_{o\_LOAD}}{2\pi \cdot C_{LOAD}} \text{ If } G_{o\_LOAD} \text{ is active then}$$

$$f_{3dB} = \frac{I_D (\lambda_{M1} + \lambda_{M2})}{2\pi \cdot C_{LOAD}} \equiv \frac{1}{R_{LOAD} \cdot 2\pi \cdot C_{LOAD}}$$

The M1 device is a voltage controlled source and the small gate voltage ( $V_{gs}$ ) creates a large current ( $I_{ds}$ ) through the  $R_{LOAD}$  creating an output voltage ( $V_o$ ) much greater than the input ( $V_{gs}$ ) ie it has voltage gain. So if you could place a low impedance current buffer between M1 and the  $R_{LOAD}$  you could greatly reduce the Miller effect – and this is exactly what M2 biased into saturation does. The resistance looking into a source is pretty low:-

$$R_{IN} = \frac{V_{IN}}{I_{IN}} = \frac{V_{gs}}{g_{M1} V_{gs}} = \frac{1}{g_{M1}} = I_D \lambda_{M2}$$


For a typical device @ 100uA,  $\lambda = 0.01$   $R_{IN} = 1E - 6\Omega$

A practical cascode amplifier is shown in Figure 2.

The device M2 acts as a low impedance current buffer, isolating the amplifying M1 with the load M3. Therefore, the gain of the cascode amplifier is approximately:-

$$A_v = \frac{gm_1}{go_3} \text{ strictly speaking } A_v = \frac{gm_1}{go_3 + go_1}$$

$$A_v = - \sqrt{\frac{2 \cdot K_{N1} \cdot W_1}{L_1 \cdot I_D \cdot \lambda_3}}$$

 

**Figure 2 Cascode amplifier with active load**

$$R_{OUT} \cong rds_3 = \frac{1}{I_D \lambda_3}$$

To be able to fully characterise the amplifier we need expressions in order to calculate output voltage swing and frequency response.

$$V_{OUTMAX} = VDD - VDS_{3SAT}$$

$$V_{OUTMIN} = \frac{\beta_{M3}}{2 \cdot \beta_{M2}} \left( VDD - VBIAS3 - |VT3| \right)^2 \left( \frac{1}{VBIAS2 - VT2} + \frac{1}{VDD - VT1} \right)$$

$$\text{Where } \beta = \frac{K \cdot W}{L}$$



### Example

Determine the gain, output resistance, gate bias voltages,  $V_{max}$  and  $V_{min}$  of the cascode amplifier of Figure 2. Assume  $W=L=1\mu m$ ,  $K_N=110\mu A/V^2$ ,  $K_P=50\mu A/V^2$ ,  $\lambda = 0.05$ ;  $V_T = 0.7V$ ,  $I_D=100\mu A$ .

The first step is to calculate the required bias voltages for each device.

First set the correct current to  $100\mu A$ , so we need to determine the correct  $v_{gs}$  to apply to the N-type FET.

$$V_{gs} = V_T + \sqrt{\frac{I_{REF}}{K_N}} = 0.7 + \sqrt{\frac{100E^{-6}}{110E^{-6}}} = 1.65V$$

$$V_{SAT} = V_{GS} - V_T = 1.65 - 0.7 = 0.95V$$

So we set the amplifying device M1 to  $v_{gs} = 1.65V$  and the second device to  $V_{gs} + V_{SAT} = 2.6V$ .

And set the correct  $V_{gs}$  to apply to the P-type FET active source.

$$V_{gs} = V_T + \sqrt{\frac{I_{REF}}{K_P}} = 0.7 + \sqrt{\frac{100E^{-6}}{50E^{-6}}} = 0.72V \text{ (apply } 5 - 0.7 = 4.3V \text{ to gate terminal)}$$

So we set the bias to M3 at  $4.3V$ .

### Calculation of gain

$$A_v = \frac{g_{m1}}{g_{o3}} \text{ strictly speaking } A_v = \frac{g_{m1}}{g_{o3} + g_{o1}}$$

$$A_v = -\sqrt{\frac{2 \cdot K_{N1} \cdot W_1}{L_1 \cdot I_D \cdot \lambda_3}} = -\sqrt{\frac{2 \cdot 110E^{-6} \cdot 1E^{-6}}{1E^{-6} \cdot 100E^{-6} \cdot 0.05}} = 6.63 = 16.5dB$$

### Output Resistance

$$R_{OUT} \cong r_{ds3} = \frac{1}{I_D \lambda_3} = \frac{1}{100E^{-6} \cdot 0.05} = 200K\Omega$$



**Output Voltage Swing**

$$V_{OUTMAX} = VDD - VDS_{3SAT}$$

$$VDS_{3SAT} = V_{GS3} - V_{T3} = 0.72 - 0.7 = 0.02V$$


$$V_{OUTMAX} = 5 - 0.02 \cong 5V$$

$$V_{OUTMIN} = \frac{\beta_{M3}}{2 \cdot \beta_{M2}} (VDD - VBIAS3 - |VT3|)^2 \left( \frac{1}{VBIAS2 - VT2} + \frac{1}{VDD - VT1} \right)$$

Where  $\beta = \frac{K \cdot W}{L}$

$$V_{OUTMIN} = \frac{\frac{50E^{-6} \cdot 1}{1}}{2 \cdot \frac{110E^{-6} \cdot 1}{1}} (5 - 3.9 - |0.7|)^2 \left( \frac{1}{2.35 - 0.7} + \frac{1}{5 - 0.7} \right) = 0.227 \cdot (0.61) \cdot (0.838) = 0.116V$$

 The ADS simulation of the example cascode is shown in Figure 4. The gain plot as a result of the simulation is shown in Figure 3.



| DC.IDS.i | DC.VSAT_N | DC.vout |
|----------|-----------|---------|
| 95.59uA  | 699.3mV   | 1.397 V |

**Figure 3 Resulting Gain plot from the ADS simulation of the example Cascode Amplifier**

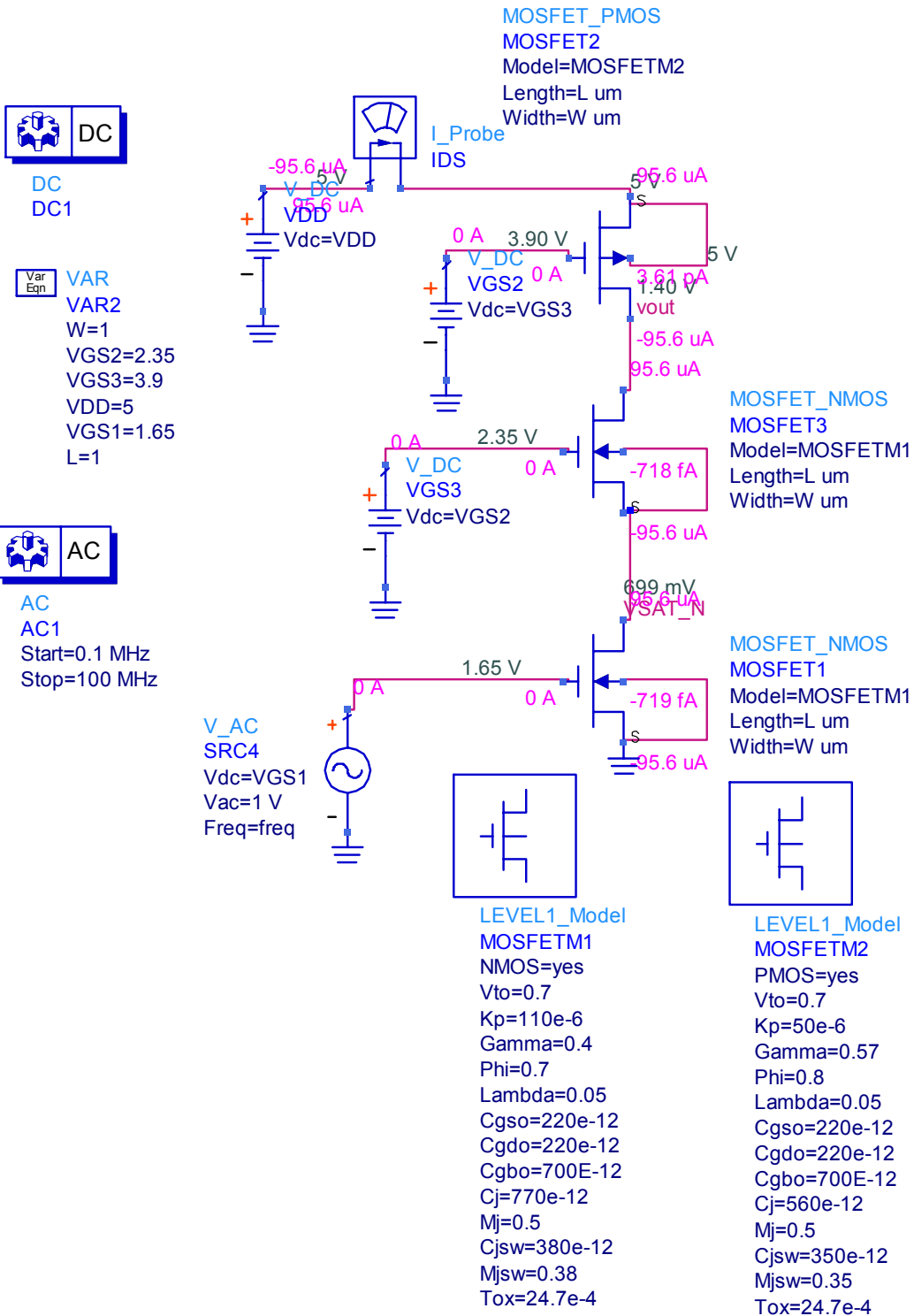
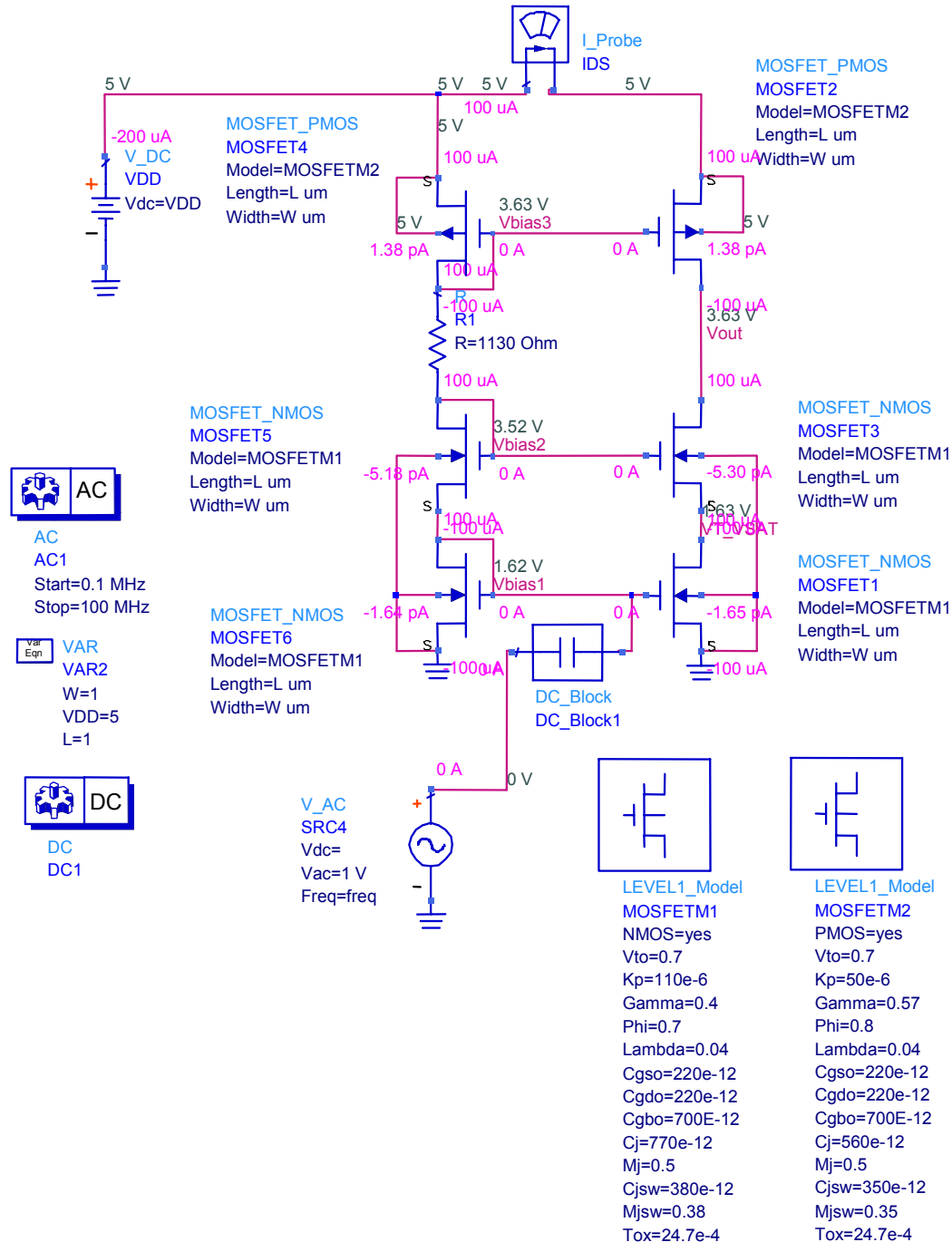


Figure 4 ADS simulation setup for the example Cascode Amplifier

A more practical circuit is shown in Figure 5. This circuit now includes the correct bias current mirrors and associated bias setting resistor. The left hand bias arm includes FETs configured as diodes such that the voltage across each source-drain is  $V_{SAT} + V_T$ . One advantage of doing

this is that the voltage drop across the resistor is smaller and therefore requires a smaller bias resistor, in this case about 1K which can easily be formed from a Polysilicate printed resistor.

 


**Figure 5 Practical Cascode Amplifier design with added bias**

The resulting plot and table of bias voltages is shown in Figure 6.



dB(AC.Vout)



| DC.IDS.i | DC.Vbias1 | DC.Vbias2 | DC.Vbias3 | DC.Vout | DC.VT_VSAT |
|----------|-----------|-----------|-----------|---------|------------|
| 99.97uA  | 1.624 V   | 3.518 V   | 3.631 V   | 3.631 V | 1.625 V    |

**Figure 6** Resulting plot from the simulation of the circuit shown in Figure 5. Note that VT+VSAT = 1.625V and closely agrees with the 1.65V calculated earlier.

We can obtain more gain from the cascode by adding a further active load as shown in Figure 7. The gain of the stage will now be:-

$$A_v = \frac{g_{m1}}{g_{o3}} \text{ strictly speaking } A_v = \frac{g_{m1}}{g_{o3} + g_{o1}} \text{ If we cascode the load then}$$

$$A_v \approx \left( \frac{g_{m1}}{g_{o3}} \right)^2 \text{ As } A_v = - \sqrt{\frac{2 \cdot K_{N1} \cdot W_1}{L_1 \cdot I_D \cdot \lambda_3}} \text{ Then the new gain} = - \left( \frac{2 \cdot K_{N1} \cdot W_1}{L_1 \cdot I_D \cdot \lambda_3} \right)$$

$$A_v \approx - \frac{2 \cdot K_{N1} \cdot W_1}{L_1 \cdot I_D \cdot \lambda_3} = - \frac{2.110E^{-6} \cdot 1E^{-6}}{1E^{-6} \cdot 100E^{-6} \cdot 0.05} = 44 = 32\text{dB}$$




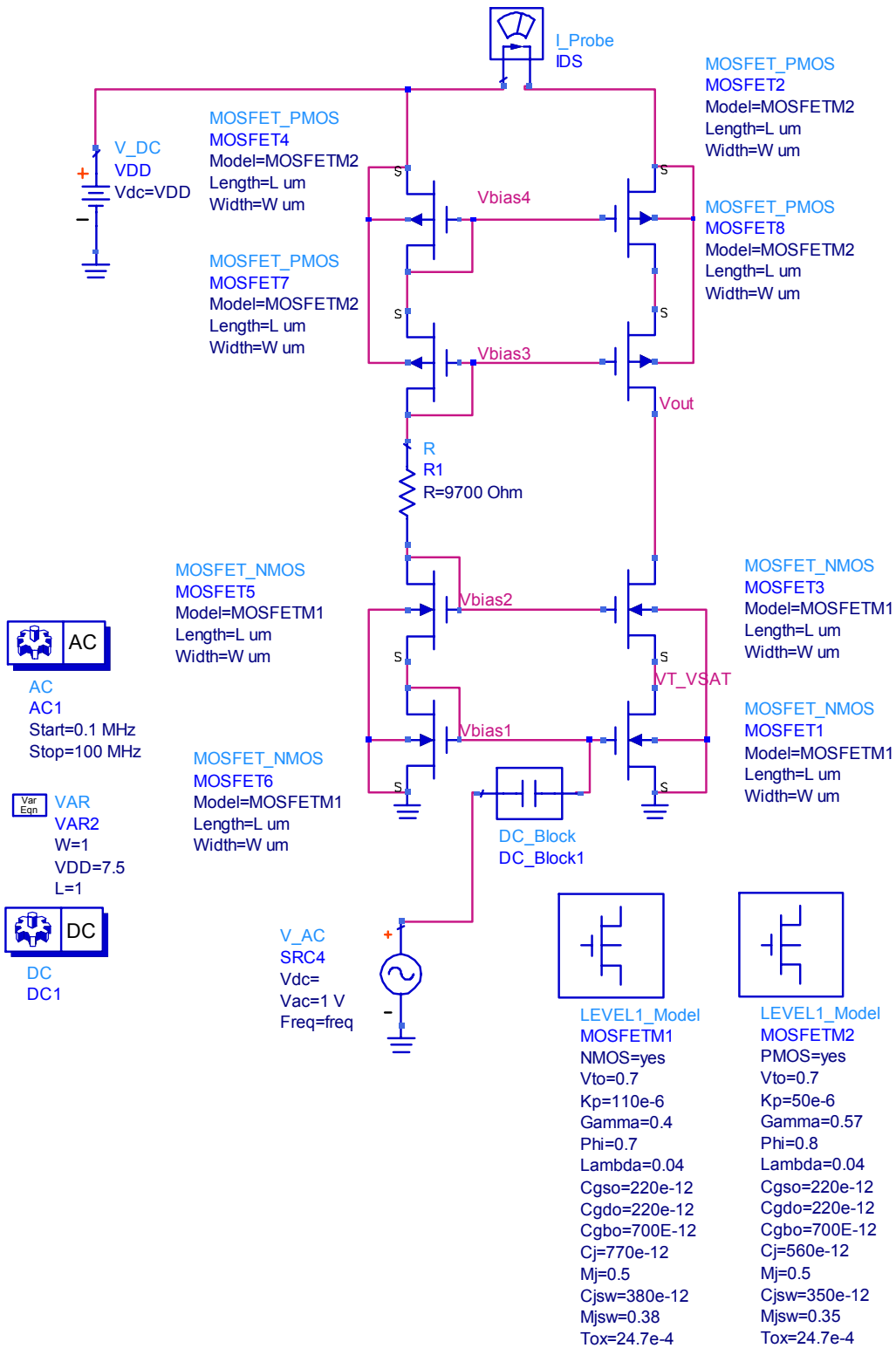


Figure 7 Addition of another active load to increase the gain of the cascode amplifier. Note however that the additional VT+VSAT has meant that to include the bias resistor the supply has been increased to 7.5V.

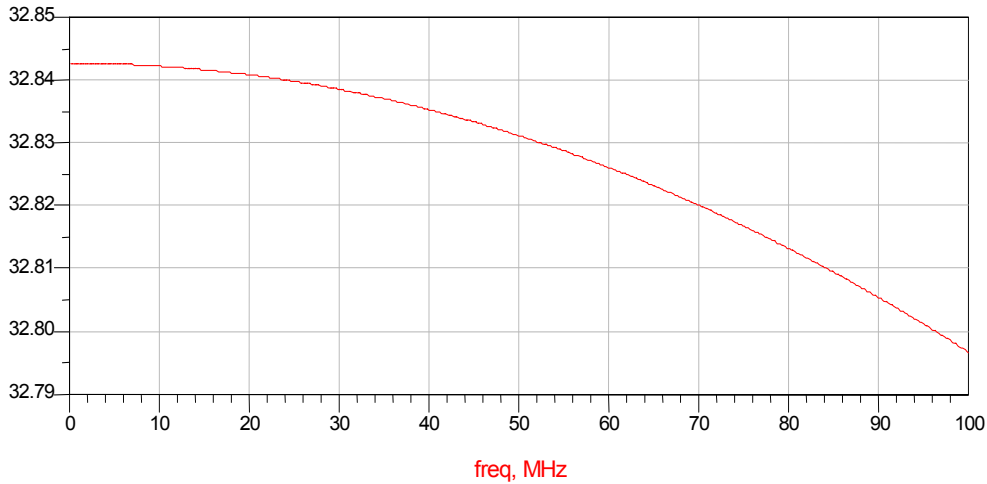

dB(AC.Vout)



| DC.IDS.i | DC.Vbias1 | DC.Vbias2 | DC.Vbias3 | DC.Vout | DC.VT_VSAT |
|----------|-----------|-----------|-----------|---------|------------|
| 101.1uA  | 1.628 V   | 3.528 V   | 4.508 V   | 4.498 V | 1.642 V    |

**Figure 8 Increased gain cascode of Figure 7, the gain of 32dB agrees with the calculation performed earlier ie  $AV \sim (gm.Ro)^2$ .**

Note one of the problems using cascode stages in that for each device we use the voltage drop across each device will be  $V_T + V_{SAT}$ . This equates to approximately 1.65V per device and with 4 devices this will cause a total voltage drop of 6.6V so we can't use our 5V rail !!! In the example the voltage supply has been increased to 7.5V to allow for the additional device.

This problem of increased voltage rail can be improved by using the folded cascode configuration, where the cascode is split between the active amp and active load and linked by another current load.

**Also we can greatly reduce  $V_{SAT}$  by increasing the W/L ratio.**

The folded cascode is very popular in the design of low voltage Op-Amps and is subject to another tutorial.

## 射频和天线设计培训课程推荐

易迪拓培训([www.edatop.com](http://www.edatop.com))由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网([www.mweda.com](http://www.mweda.com)),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



### 射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

### ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



### HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

## CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



## HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

## 13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



### 我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

### 联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>