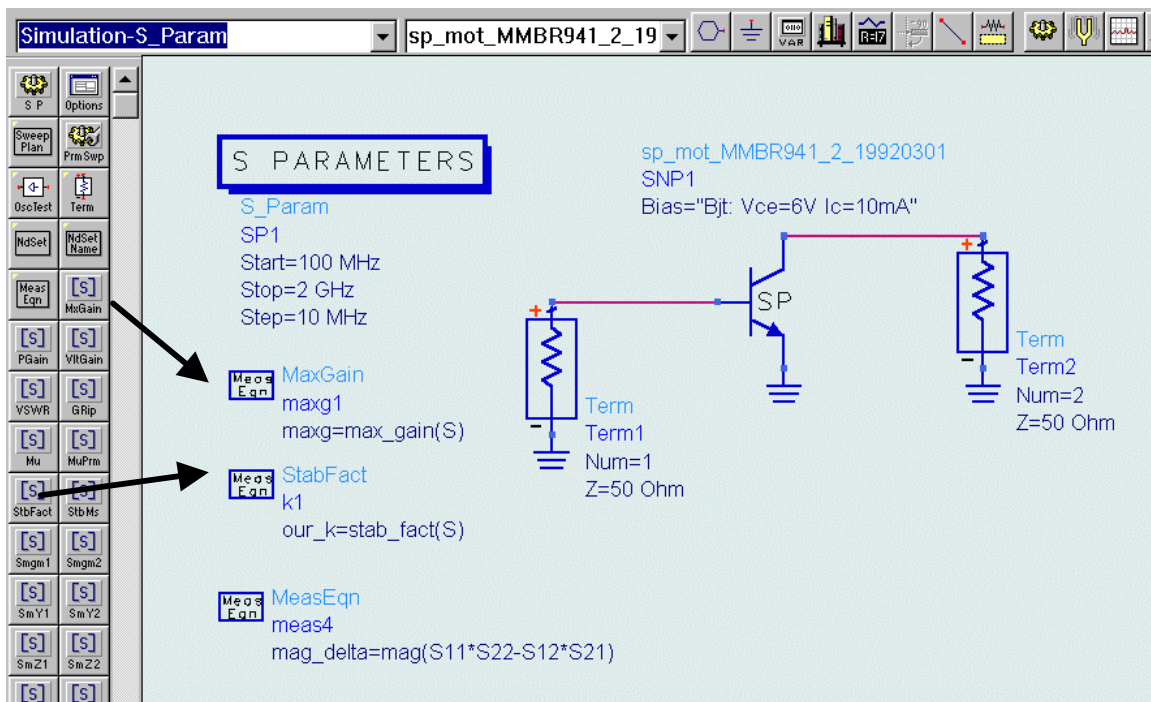


ADS Tutorial Stability and Gain Circles EEE 194RF

The first step in designing the amplifier with the S parameter method is to determine whether the amplifier is unconditionally stable or potentially unstable. This can be easily estimated using the K stability factor and delta. The amplifier will be unconditionally stable if:



$$K > 1 \text{ and } \text{mag}(\Delta) < 1.$$

These factors are easily calculated using Measurement Equations in the ADS schematic panel. K is pre-programmed in as stab_fact which can be selected from the S-parameter palette on the left. Delta can be programmed yourself using a blank MeasEqn. The maximum available gain (MAG) and maximum stable gain (MSG) can also be calculated using the max_gain function.




When swept over a range of frequencies, it can be clearly seen where the device will be unconditionally stable (above 1.5 GHz for this example). Note that the user-defined equation capability of the display panel is used to also calculate and plot MSG and the intrinsic transducer gain (GT_i) with both Γ_S and $\Gamma_L = 0$. In the regions where $K < 1$, the max_gain function plots MSG. When unconditionally stable, it plots MAG.

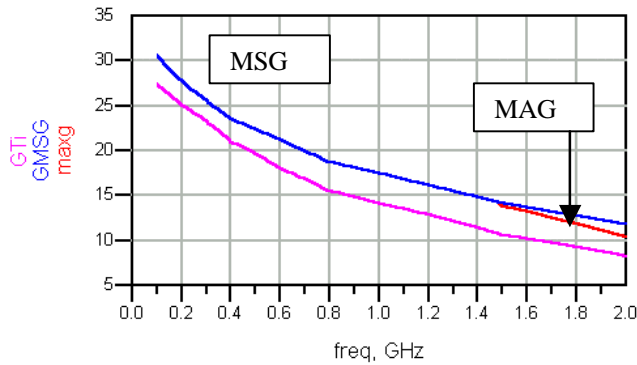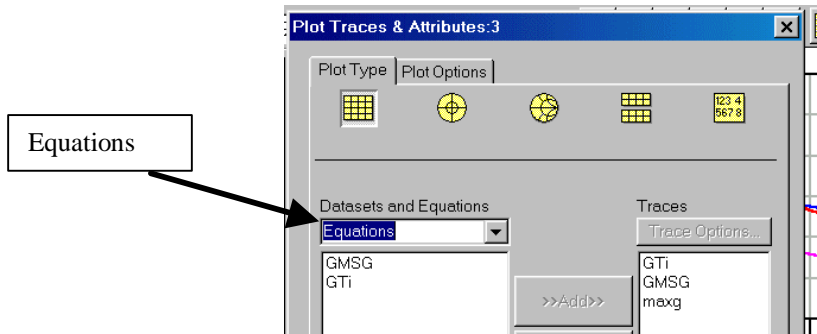ADS tip: When you want to plot from your user-defined equations, you need to select the equations dataset in the plotting panel.



Eqn $GMSG=10*\log(\text{mag}(S21)/\text{mag}(S12))$

Eqn $GTi=20*\log(\text{mag}(S21))$

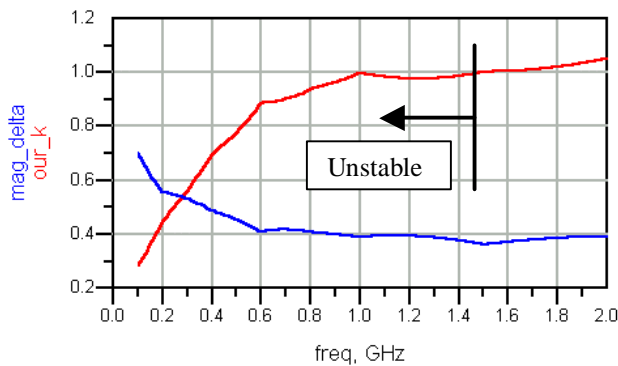

Next, you could check (as the book suggests) to see if the device is unilateral. (this is rarely the case). Evaluate the Unilateral Figure of Merit, U, at the design frequency using a Measurement Equation. Let's choose 500 MHz for our example.

```

MeasEqn Unilateral Figure of Merit
meas1
U=(mag(S12)*mag(S21)*mag(S11)*mag(S22))/((1-(mag(S11))**2)*(1-(mag(S22))**2))

MeasEqn meas2
UFM_minus=10*log(1/((1+U)**2))

MeasEqn meas3
UFM_plus=10*log(1/((1-U)**2))

```

Show the result in a table in the display panel.

freq	U	UFM_minus	UFM_plus
500.0MHz	0.137	-1.114	1.278


Here, we see that at 500 MHz, the device is clearly not unilateral. The unilateral approximation would have an error of over 1 dB.

Bilateral design. If the device is unconditionally stable at the design frequency, then the input and output can be conjugately matched as shown in Section 3.6 of Gonzalez. Γ_{MS} and Γ_{ML} can be determined uniquely. The input and output VSWR would = 1 in this case. This would be applicable for this device in the region where $K > 1$. The conjugate match reflection coefficients can be calculated on ADS using the Smgm1 and Smgm2 measurement equation icons in the S-parameter palette.

However, at 500 MHz, we find that $K = 0.75$. We must take into account stability as well as gain. It is wise to design the amplifier for less than the MSG to allow margin for stability. In this case, we need a systematic design method, because changes in Γ_S will affect Γ_{OUT} and changes in Γ_L will affect Γ_{IN} .


The operating power gain, G_P , provides a graphical design method suitable for bilateral amplifiers. Gain circles can be calculated that show contours of constant operating power gain. G_P is useful since it is independent of the source impedance; the gain circle represents the gain what would be obtained if a magic genie adjusted $\Gamma_S = \Gamma_{IN}^*$ for each value of Γ_L on the circle. Then, $G_P = G_T$, ie. the operating power gain equals the transducer gain. Let's illustrate.

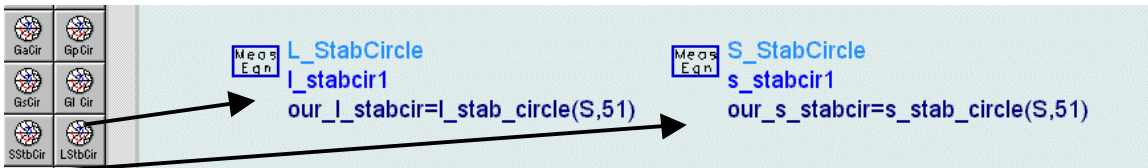Since we will need to evaluate the load plane for stability, so stability circles should also be calculated. This is done by using the LstbCir function. Source stability circles should also be calculated.



I have found it more convenient to calculate the operating power gain circles on the data display rather than on the schematic. On the data display, you can change the gain values without having to resimulate the amplifier. Use the Eqn function to write gain circle equations. The syntax is: `gp_circle(S, gain, # points on circle)` where S is the S-parameter matrix. In the example below, the gain circles at MSG, and 1 and 2 dB below MSG are plotted. A marker is placed on the -2 dB circle. Γ_L can be read off the display as magnitude = 0.057 with angle = 22 degrees. If the input is conjugately matched (and stable), then the gain should be $\text{maxg} - 2 = 20.4$ dB.

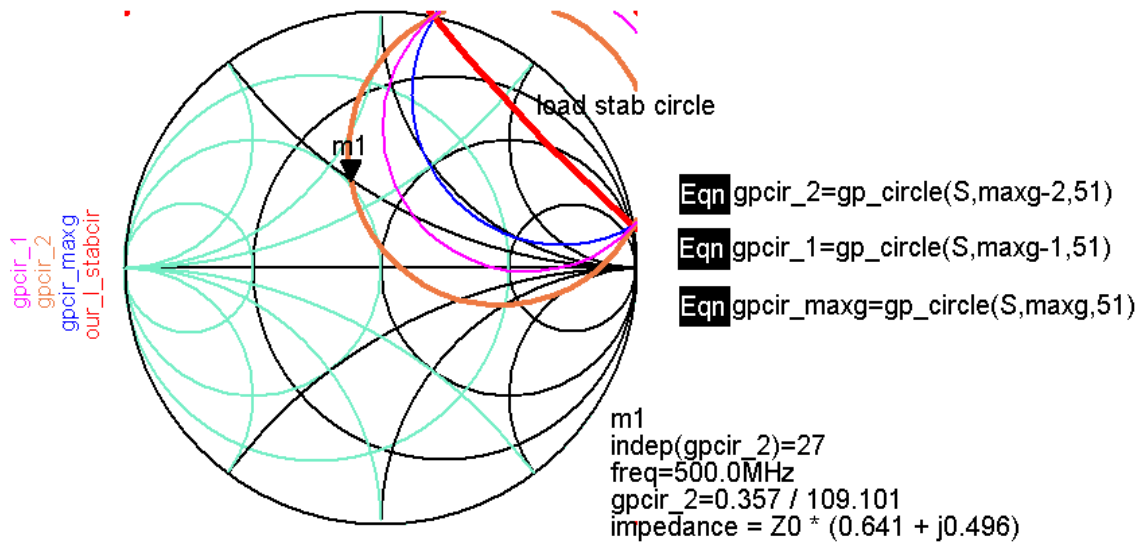
The load stability circle is also shown. The load impedance can be chosen away from this circle to maximize stability.




Next, calculate the input reflection coefficient for your choice of Γ_L and make sure it is stable. To do this, plot the source plane stability circle and compare with Γ_{IN} . You can use the marker (m2) to compare values of the source stability circle reflection coefficient with γ_{IN} . We can see that this choice will be stable at the design frequency.

$\text{Eqn } \gamma_{L} = m1[0]$ $\text{Eqn } \gamma_{S} = \text{conj}(\gamma_{IN})$
 $\text{Eqn } \gamma_{IN} = S_{11} + (S_{12} * S_{21} * \gamma_{L}) / (1 - S_{22} * \gamma_{L})$


γ_{IN}	γ_{S}	γ_{L}
0.486 / -91.799	0.486 / 91.799	0.357 / 109.101

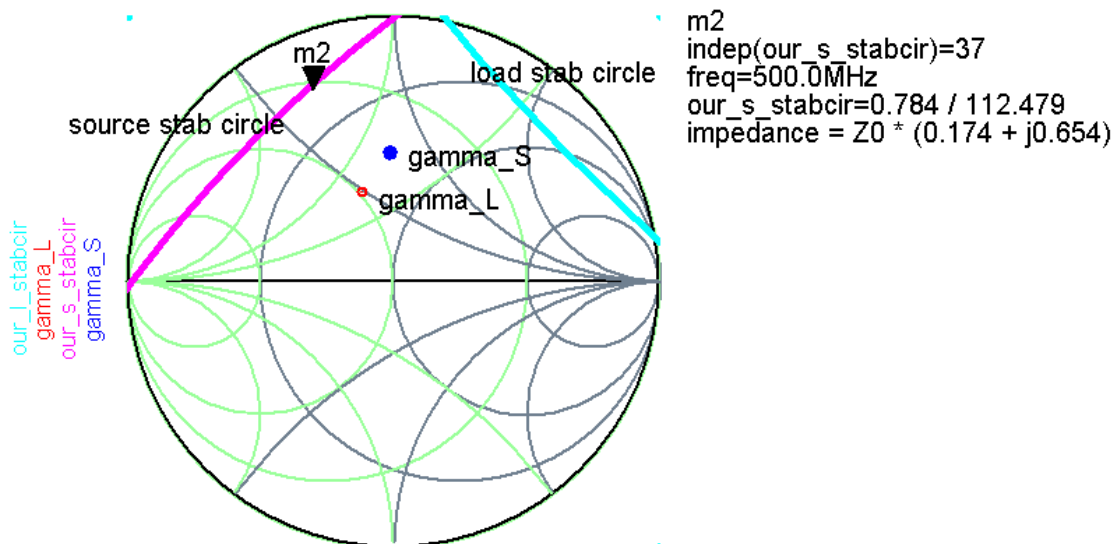

Biasing and matching network design. The next step in designing the amplifier will be the implementation of the input and output matching networks such that they provide reflection coefficients Γ_S and Γ_L as determined above. This can be done using the Smith chart. In general, there may be several solutions possible using lumped or distributed L networks. In selecting a design, you need to consider how you will bias the amplifier. You have 2 choices: bias with RF chokes and blocking capacitors or bias through the matching network elements.

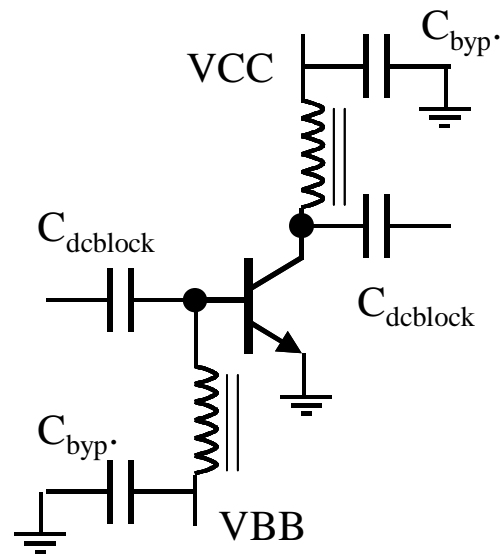

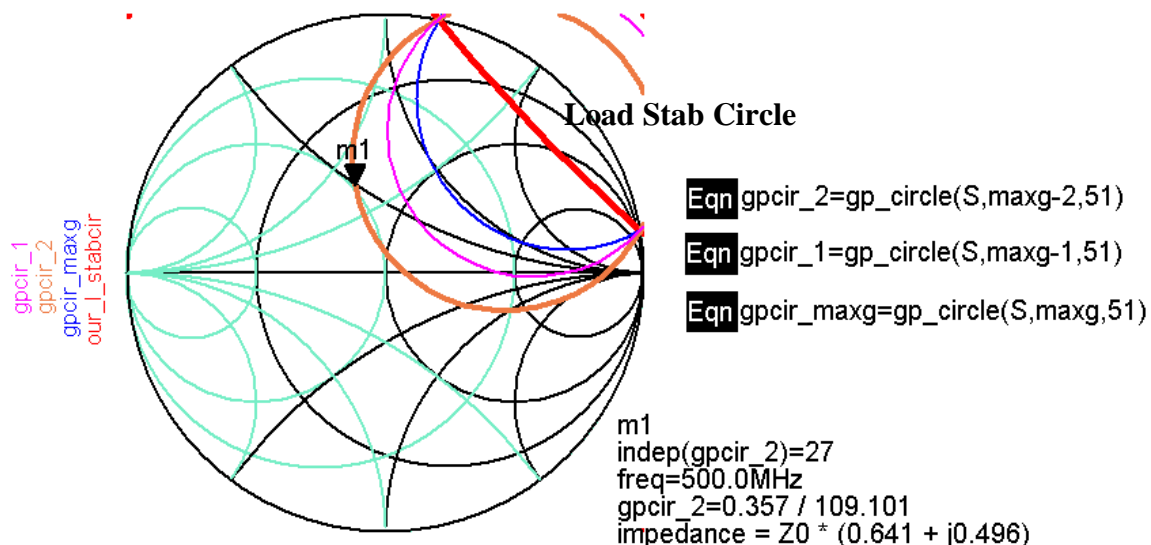
When possible, biasing through the matching network will often minimize the number of components and may prove to be easier to implement. Consider the load plane.




The marker is on the -2 dB operating power gain circle and represents our choice of Γ_L . Notice that we have many options for Γ_L as long as we keep a respectable distance from the load stability circle. As shown above, if we choose a Γ_L at the location of m1, we are on the unit constant conductance circle ($g=1$). Adding a shunt inductance across the 50

ohm load will place us at m1. The shunt inductance can be implemented with a shorted transmission line stub. This stub can also serve as our bias port if we are careful to provide appropriate bypass capacitance for the power supply.

gamma_IN	gamma_S	gamma_L
0.486 / -91.799	0.486 / 91.799	0.357 / 109.101

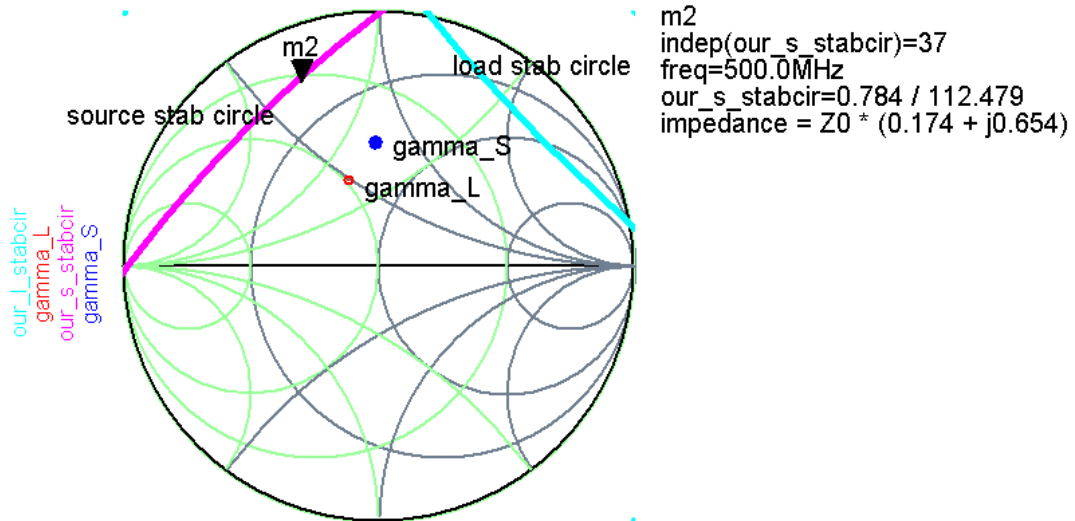

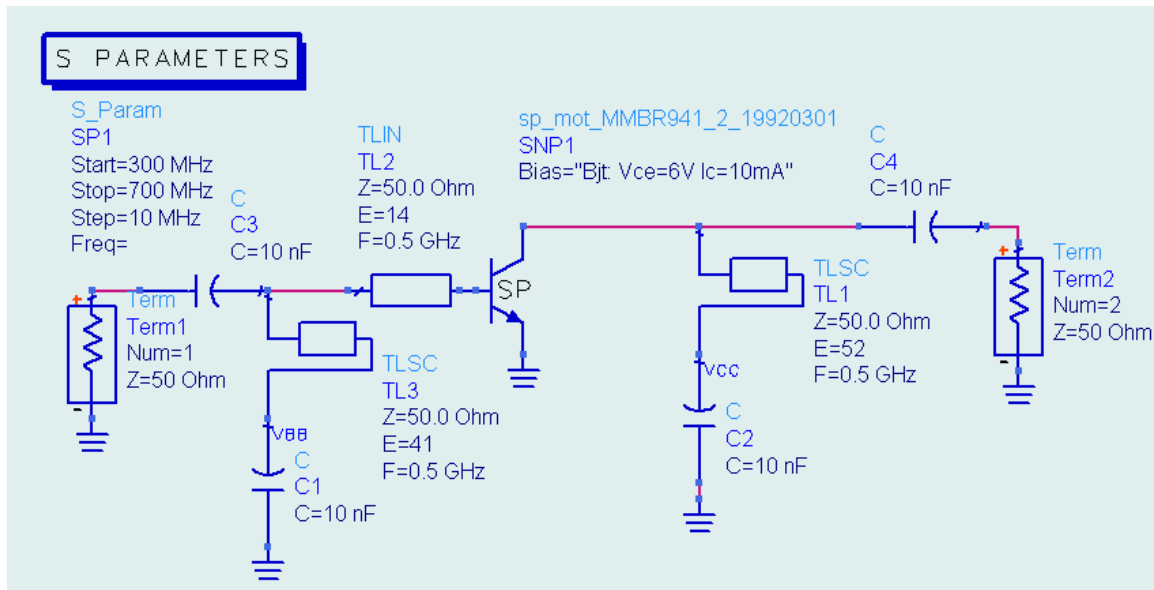We can use the same idea for the source plane: add shunt inductance, moving up the $g=1$ circle. Then add a series 50 ohm transmission line until you reach Γ_S . The complete circuit looks like this:





The capacitors are needed for bypassing and DC blocking. If we simulate this amplifier at the design frequency, it produces the expected gain of 20.3 dB. Although the K factor is less than 1, S11 and S22 both have magnitudes less than 1 which implies that the amplifier will be stable. We have a good input match as expected.



freq	our_k	GP	S(2,2)	S(1,1)
500.0MHz	0.779	20.343	0.659 / 32....	0.022 / 86....

$$\text{Eqn GP} = 20 * \log(\text{mag}(S_{21}))$$

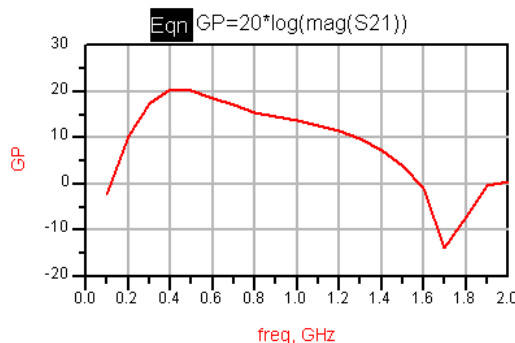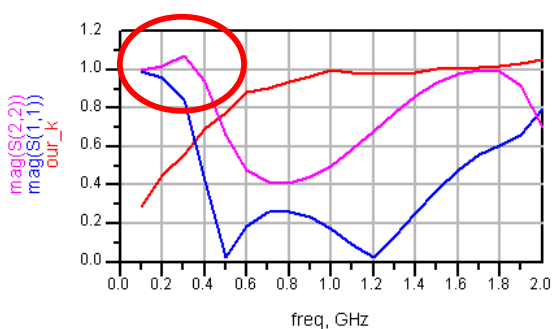Wideband Stability. We must also guarantee that the amplifier is stable not only at the design frequency but everywhere else as well. To do this, we will sweep the frequency over a wide range (100 MHz to 2 GHz) and look at S11 and S22. Here, we can see that S22 is greater than 1 at 300 MHz. We must modify the circuit to prevent this.



We could simulate the transistor again at 300 MHz and look at stability circles. Then, if you simulate the matching networks at this frequency to find Γ_S and Γ_L , it turns out that Γ_S is beyond the stability circle boundary. We could try a different Γ_L and test again. But, we may be able to solve the problem directly. Notice that the matching networks both have shunt lines that become short circuits at low frequencies. The device may become unstable as we approach Γ_L or $\Gamma_S = 1$. So, add some small series resistance to these shunt stubs to modify the low frequency behavior. Fortunately, this works in this case. Adding 5 ohms in series with each stub costs about 1 dB of gain, but keeps $\text{mag}(S_{22}) < 1$ at all frequencies.

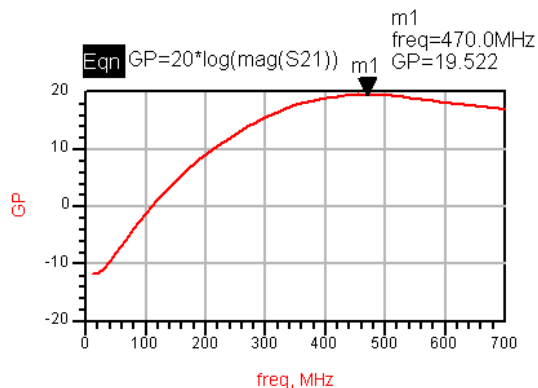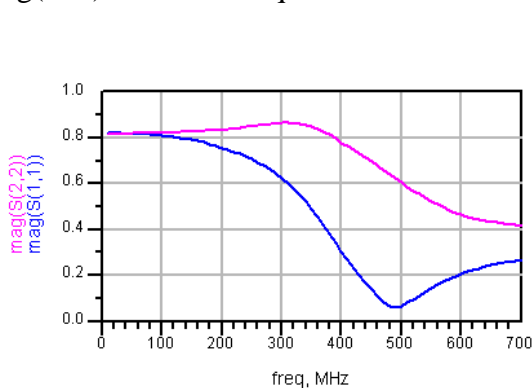


Other alternatives for stabilization would include adding the stabilizing resistor at the device using the stability circle technique at 300 MHz, or possibly choosing a different

Γ_L value to start with might produce a stable design. You can see that the wideband stabilization of an amplifier can involve some effort in design.

If RF chokes were used for biasing instead of the matching network approach, we would need to model the RFC as an equivalent RLC network and determine stability of the amplifier over a wide frequency range as well.

Our final design looks like this:

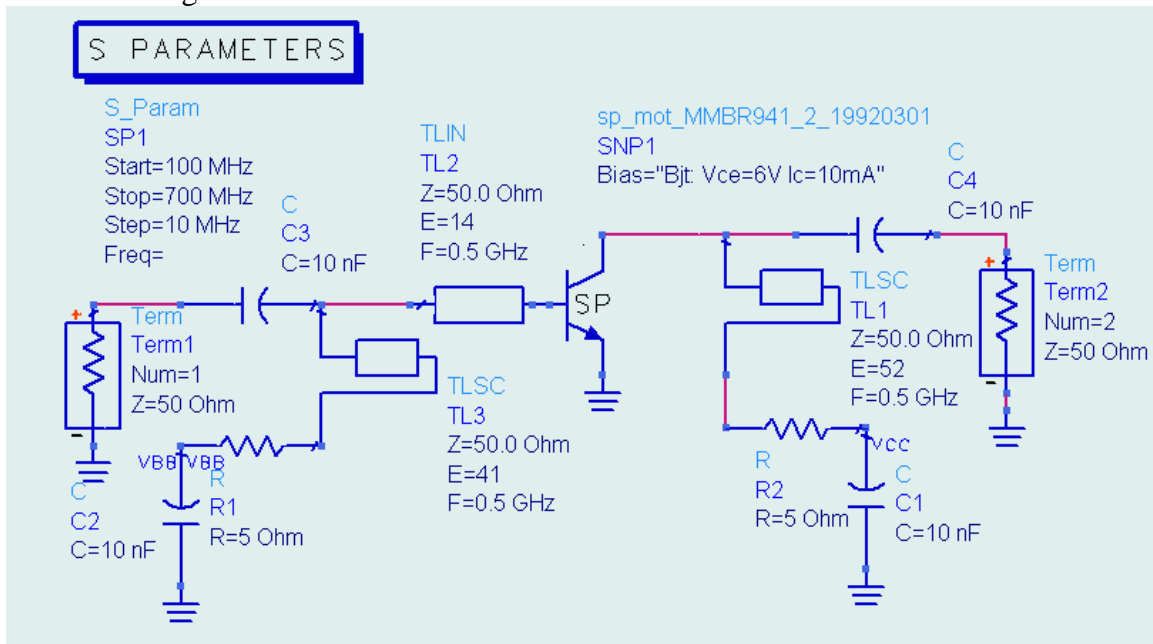

A suitable bias control circuit will now be needed to maintain the correct VCE and IC values for the amplifier. Note that constant VBE or constant IB designs are not acceptable because of the exponential temperature dependence of IC on VBE and because of the large temperature coefficient of β (0.7%/degree C).

射频和天线设计培训课程推荐

易迪拓培训(www.edatop.com)由数名来自于研发第一线的资深工程师发起成立,致力并专注于微波、射频、天线设计研发人才的培养;我们于 2006 年整合合并微波 EDA 网(www.mweda.com),现已发展成为国内最大的微波射频和天线设计人才培养基地,成功推出多套微波射频以及天线设计经典培训课程和 ADS、HFSS 等专业软件使用培训课程,广受客户好评;并先后与人民邮电出版社、电子工业出版社合作出版了多本专业图书,帮助数万名工程师提升了专业技术能力。客户遍布中兴通讯、研通高频、埃威航电、国人通信等多家国内知名公司,以及台湾工业技术研究院、永业科技、全一电子等多家台湾地区企业。

易迪拓培训课程列表: <http://www.edatop.com/peixun/rfe/129.html>



射频工程师养成培训课程套装

该套装精选了射频专业基础培训课程、射频仿真设计培训课程和射频电路测量培训课程三个类别共 30 门视频培训课程和 3 本图书教材;旨在引领学员全面学习一个射频工程师需要熟悉、理解和掌握的专业知识和研发设计能力。通过套装的学习,能够让学员完全达到和胜任一个合格的射频工程师的要求...

课程网址: <http://www.edatop.com/peixun/rfe/110.html>

ADS 学习培训课程套装

该套装是迄今国内最全面、最权威的 ADS 培训教程,共包含 10 门 ADS 学习培训课程。课程是由具有多年 ADS 使用经验的微波射频与通信系统设计领域资深专家讲解,并多结合设计实例,由浅入深、详细而又全面地讲解了 ADS 在微波射频电路设计、通信系统设计和电磁仿真设计方面的内容。能让您在最短的时间内学会使用 ADS,迅速提升个人技术能力,把 ADS 真正应用到实际研发工作中去,成为 ADS 设计专家...



课程网址: <http://www.edatop.com/peixun/ads/13.html>



HFSS 学习培训课程套装

该套课程套装包含了本站全部 HFSS 培训课程,是迄今国内最全面、最专业的 HFSS 培训教程套装,可以帮助您从零开始,全面深入学习 HFSS 的各项功能和在多个方面的工程应用。购买套装,更可超值赠送 3 个月免费学习答疑,随时解答您学习过程中遇到的棘手问题,让您的 HFSS 学习更加轻松顺畅...

课程网址: <http://www.edatop.com/peixun/hfss/11.html>

CST 学习培训课程套装

该培训套装由易迪拓培训联合微波 EDA 网共同推出,是最全面、系统、专业的 CST 微波工作室培训课程套装,所有课程都由经验丰富的专家授课,视频教学,可以帮助您从零开始,全面系统地学习 CST 微波工作的各项功能及其在微波射频、天线设计等领域的设计应用。且购买该套装,还可超值赠送 3 个月免费学习答疑...

课程网址: <http://www.edatop.com/peixun/cst/24.html>



HFSS 天线设计培训课程套装

套装包含 6 门视频课程和 1 本图书,课程从基础讲起,内容由浅入深,理论介绍和实际操作讲解相结合,全面系统的讲解了 HFSS 天线设计的全过程。是国内最全面、最专业的 HFSS 天线设计课程,可以帮助您快速学习掌握如何使用 HFSS 设计天线,让天线设计不再难...

课程网址: <http://www.edatop.com/peixun/hfss/122.html>

13.56MHz NFC/RFID 线圈天线设计培训课程套装

套装包含 4 门视频培训课程,培训将 13.56MHz 线圈天线设计原理和仿真设计实践相结合,全面系统地讲解了 13.56MHz 线圈天线的工作原理、设计方法、设计考量以及使用 HFSS 和 CST 仿真分析线圈天线的具体操作,同时还介绍了 13.56MHz 线圈天线匹配电路的设计和调试。通过该套课程的学习,可以帮助您快速学习掌握 13.56MHz 线圈天线及其匹配电路的原理、设计和调试...

详情浏览: <http://www.edatop.com/peixun/antenna/116.html>



我们的课程优势:

- ※ 成立于 2004 年,10 多年丰富的行业经验,
- ※ 一直致力并专注于微波射频和天线设计工程师的培养,更了解该行业对人才的要求
- ※ 经验丰富的一线资深工程师讲授,结合实际工程案例,直观、实用、易学

联系我们:

- ※ 易迪拓培训官网: <http://www.edatop.com>
- ※ 微波 EDA 网: <http://www.mweda.com>
- ※ 官方淘宝店: <http://shop36920890.taobao.com>